



The Basics of Linear Regulator and Switching Regulator

AGENDA

1. Linear Regulator Basics

- Operating Principles
- Types and Circuit Configuration
- Advantages vs Disadvantages, and Applications
- Important Specifications
- Efficiency and Thermal Calculation


2. Switching Regulator Basics

- Types of Switching Regulator
- Advantages vs Disadvantages, and Comparison with Linear Regulator
- Operating Principles of Buck Converter
- Differences between Synchronous and Nonsynchronous Rectifying
- Efficiency Improvements at Light Load for the Synchronous Converter
- Control Methods (Voltage Mode, Current Mode, Hysteresis Control)
- Protective and Sequencing Functions
- Considerations on Switching Frequencies

1. Linear Regulator Basics

- Operating Principles
- Types and Circuit Configuration
- Advantages vs Disadvantages, and Applications
- Important Specifications
- Efficiency and Thermal Calculation


Operating Principles of Linear Regulator

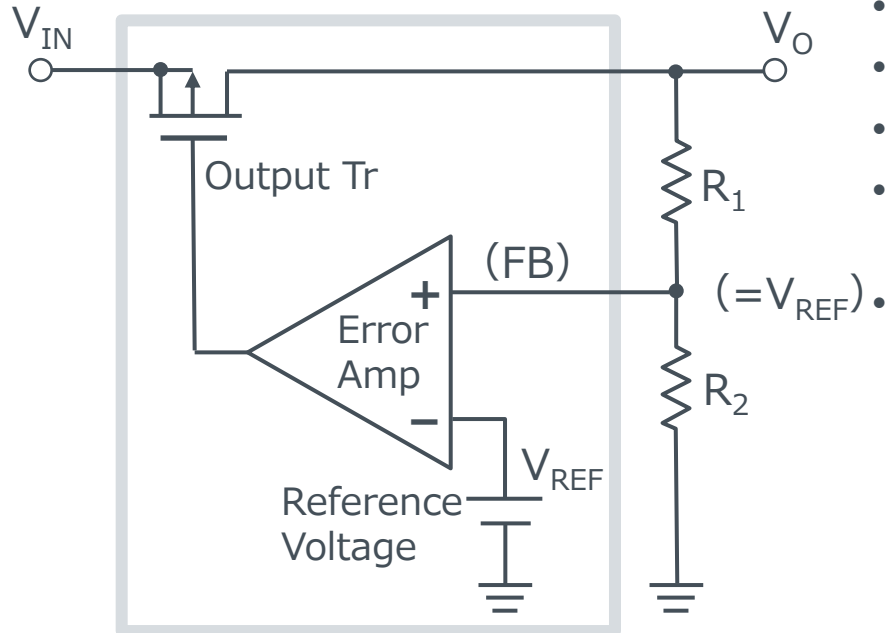

- Composed of an error amp, a voltage reference, and an output transistor
- Same operation as an inverting amp
- V_{OUT} is set by the ratio between R_1 and R_2 , because the voltage of non-inverting input is equal to V_{REF}

$$V_O = \frac{V_{REF}}{R_2} \times (R_1 + R_2)$$
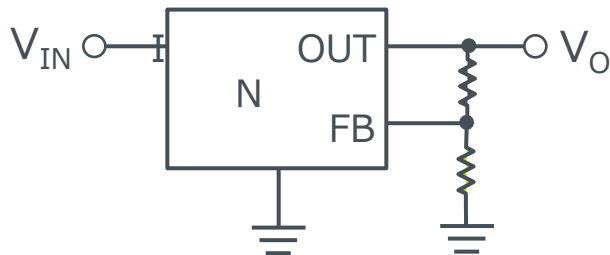
$$= \frac{R_1 + R_2}{R_2} \times V_{REF}$$



EX: $V_{REF} = 1.0V$, $V_O = 3.3V$, $R_2 = 10k\Omega$

$$3.3V = \underbrace{\frac{1.0V}{10k\Omega}}_{100\mu A} \times (R_1 + 10k\Omega)$$

$$100\mu A \times 33k\Omega = 3.3V \quad \text{Therefore } R_1 = 23k\Omega$$

Types of Linear Regulator

Linear Regulators


- | | |
|--|-------------------------|
| • Positive Voltage
(Fixed/Adjustable) | - Conventional
- LDO |
| • Negative Voltage
(Fixed/Adjustable) | - Conventional
- LDO |

- Naming of linear regulator: Series regulator, 3-terminal regulator,
- Dropper, or LDO
- LDO is a modification to 1V or less of a conventional dropout
- Adjustable types require the output setting resistors, as opposed to that fixed output types include the resistors
- Generally, bipolar process linear regulators have higher voltage tolerant than CMOS, but the supply current is larger than CMOS
- Package type is various and low-thermal-resistance is required



Circuit Configuration of Linear Regulator

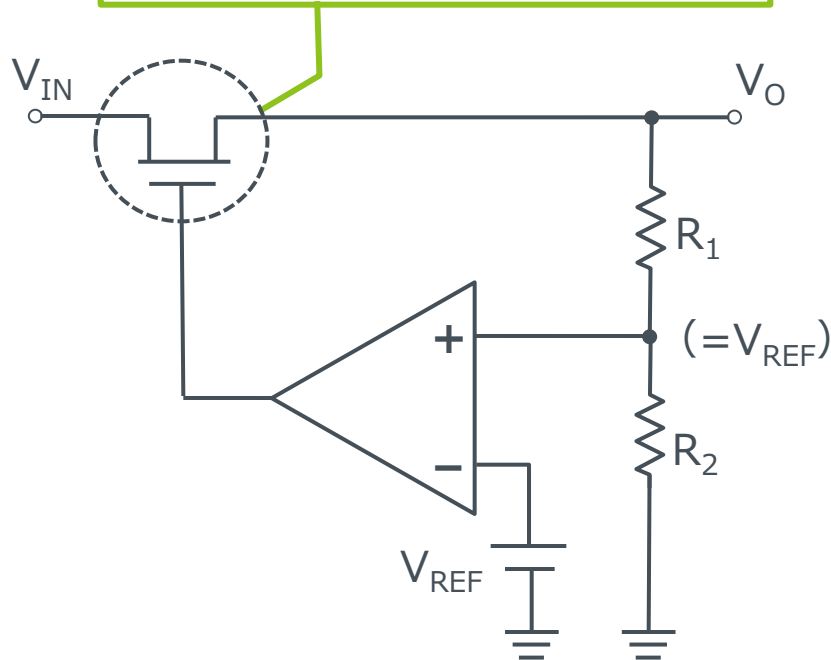For the control transistor, bipolar NPN/PNP transistor or Pch/Nch MOSFET with varying dropout voltages and performance characteristics is used.



- Dropout voltages vary with the type of the control transistor
- But operating principles as basically same
- NPN conventional configuration is used for 0.5A to 1A regulators like 78xx/79xx
- NPN LDO can supply larger I_{out} than 5A.
- PNP LDO is a standard of LDO
- Pch/Nch MOSFET achieves lower dropout voltage than PNP LDO

Control Transistor	Dropout Voltage
NPN Conventional	Approx. 3V
NPN LDO	1V~2V
PNP LDO	0.5V or less
MOSFET LDO	0.5V or less

Advantages vs Disadvantages, and Applications

Advantages


- ✓ Simplicity of design
- ✓ Lower parts count
- ✓ Space savings (unless a heat sink is used)
- ✓ Low noise
- ✓ Fast transient response
- ✓ Low cost

Disadvantages

- ✓ Low efficiency if input-output difference is large
- ✓ Low efficiency = significant heat dissipation
- ✓ May require a heat sink
- ✓ Capable exclusively of step-down operations

Applications

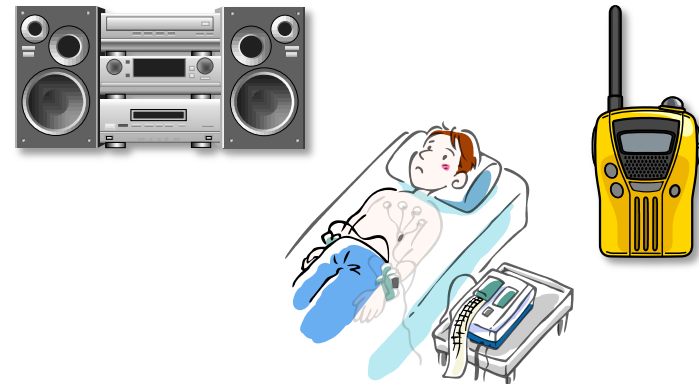- AV devices
- RF, radio, communication devices
- Medical equipment
- Measurement devices
- Small-power supply



Important Specifications of Linear Regulator

- ✓ Input voltage range
- ✓ Output voltage range
- ✓ Output (VREF) accuracy
- ✓ Output current
- ✓ Dropout voltage
- ✓ Transient response characteristics
- ✓ Ripple rejection ratio

Basic Verification Points in a Data Sheet

- Always check the absolute maximum rating
- Verify temperature and voltage conditions (Do they represent real-life conditions?)
- Using a graph, verify continuous characteristics beyond guaranteed values
- Determine which value, Typ, Min, or Max, must be used as a starting point


Example table of specifications

● **Electrical Characteristics** (Unless otherwise noted, $T_a=25^{\circ}\text{C}$, $V_{\text{EN}}=3\text{V}$, $V_{\text{CC}}=3.3\text{V}$, $R_1=16\text{k}\Omega$, $R_2=7.5\text{k}\Omega$)

Parameter	Symbol	Limits			Unit	Conditions
		Min.	Typ.	Max.		
Circuit current at shutdown mode	I_{SD}	-	0	5	μA	$V_{\text{EN}}=0\text{V}$, OFF mode
Bias current	I_{CC}	-	250	500	μA	
Line regulation	Reg. I	-1	-	1	%	$V_{\text{CC}}=(V_0+0.6\text{V})\rightarrow 5.5\text{V}$
Load regulation	Reg. I_O	-1.5	-	1.5	%	$I_O=0\rightarrow 0.5\text{A}$
Minimum dropout voltage1	V_{CO1}	-	0.1	0.15	V	$V_{\text{CC}}=3.3\text{V}$, $I_O=125\text{mA}$
Minimum dropout voltage2	V_{CO2}	-	0.2	0.30	V	$V_{\text{CC}}=3.3\text{V}$, $I_O=250\text{mA}$
Minimum dropout voltage3	V_{CO3}	-	0.3	0.45	V	$V_{\text{CC}}=3.3\text{V}$, $I_O=375\text{mA}$
Minimum dropout voltage4	V_{CO4}	-	0.4	0.60	V	$V_{\text{CC}}=3.3\text{V}$, $I_O=500\text{mA}$
Output reference voltage(Variable type)	V_{FB}	0.792	0.800	0.808	V	$I_O=0\text{A}$

Important Specifications of Linear Regulator


- Input Voltage Range
 - Meaning: A voltage that may be applied to the input terminal
 - Check if input voltage range guarantees adequate operation or fulfillment of specifications, or if it is a maximum rating value
 - Normally comply with the recommended conditions
 - Minimum operating input voltage is $V_o + \text{dropout voltage}$ or higher.
 - Due to $T_{j_{MAX}}$ factor, the input voltage range is limited by V_o , I_o , and T_a conditions
- Output Voltage Range
 - Meaning: Range of output voltages (a fixed value for the fixed type)
 - V_{REF} to $(V_{INMAX} - V_{DROPOUT})$
 - Normally comply with the recommended range
 - Due to $T_{j_{MAX}}$ factor, the output range is subject to limits by V_o , I_o , and T_a conditions
- Output accuracy (V_{REF} accuracy)
 - Meaning: the extent of error indicated by $\pm \%$
 - For the fixed type, a fixed value (V_o); for the adjustable type, V_{REF}

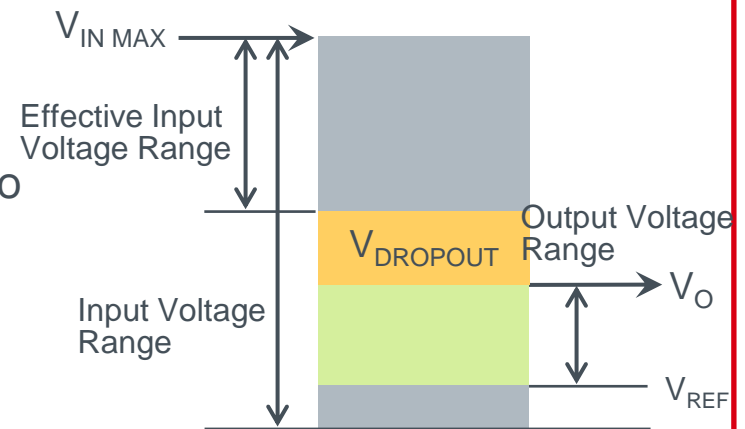

Important Specifications of Linear Regulator

● Output Current

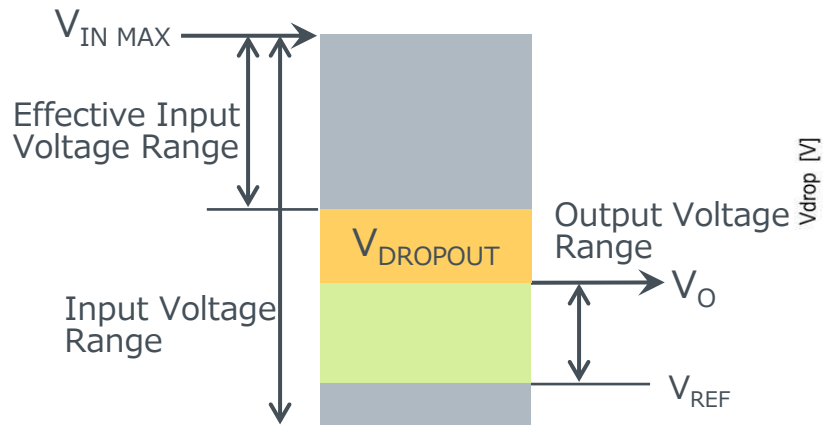
- Meaning: A current that can be output (capability)
- The expression current limit is also used in some cases
- Caution: Make sure if the term refers to a maximum or minimum value
- Any specifications on short-circuit current should also be considered
- Due to $T_{j\text{MAX}}$, output current is subject to limits by V_O , I_O , and T_a



● Dropout Voltage

- Meaning: Voltage difference between input and output necessary to regulate the output
- Also referred to as input/output voltage difference or loss voltage
- If the difference is further reduced, the regulator ceases to operate
- The LDO has a small dropout voltage

VDROPOUT vs I_O , T_a


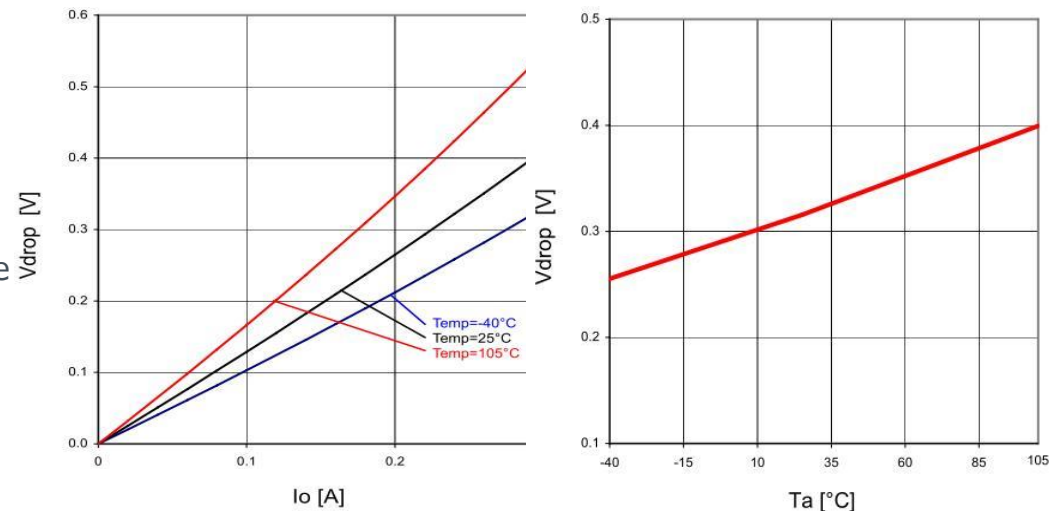


Important Specifications of Linear Regulator

● Transient Response Characteristics

- Meaning: Time to settle the fluctuations of an V_{OUT} by rapid load current changes
- Load current changes occur such when a large-power load (ex CPU) wakes up
- Must be considered separately from a shift in output voltage due to continuous increase and decrease in load.
- Basically there are no specification values; transient response characteristics must be verified in terms of a graph.
- Transient response characteristics are affected not only by the IC performance but also by the output capacitance (of the capacitor).

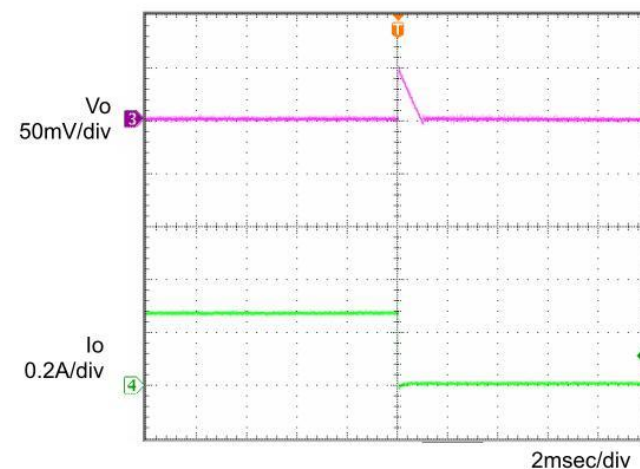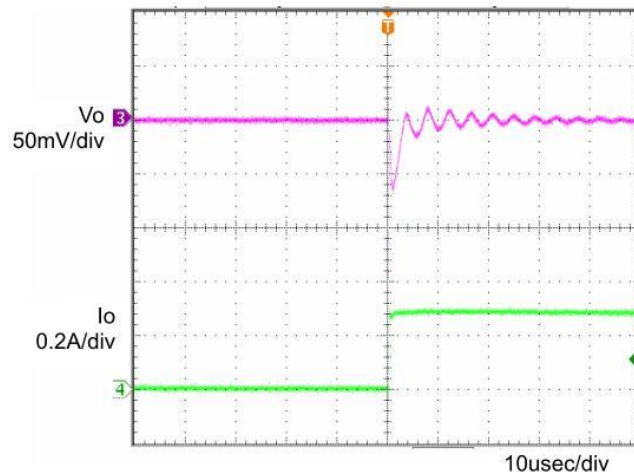Example of Transient Response Characteristics





Important Specifications of Linear Regulator

● Ripple Rejection Ratio

- Meaning: The percentage of ripples (pulsation) contained in the input voltage that is rejected from the output voltage. Expressed as dB in most cases
- Also called PSRR (power supply voltage ripple rejection) or input voltage ripple rejection, they refer to the same thing
- Note that the rejection ratio depends on the ripple frequency
- If the linear regulator is used as a post regulator of the switching regulator, the ripple rejection capability can reduce the output ripple of switching regulator when rectification and smoothing of the switching regulator are not sufficient

Example of Ripple Rejection Ratio

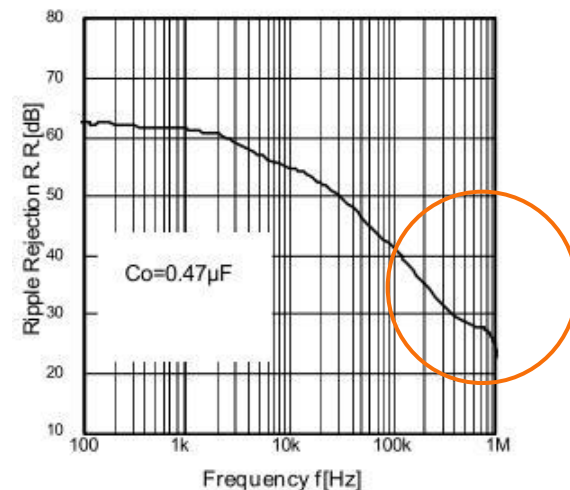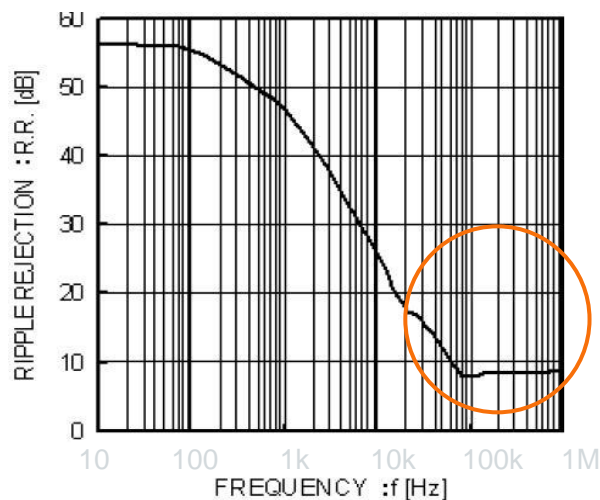

Efficiency and Thermal Calculation

◆ Definition for Efficiency

- Efficiency = $\frac{\text{Output Power}}{\text{Input Power}} \times 100$ (%)
 - Input Power = $V_{IN} \times I_{IN}$ Where: $I_{IN} = I_O + I_{CC}$
 - Output Power = $V_O \times I_O$


EX: $V_{IN} = 5V$, $V_O = 3.3V$, $I_O = 0.2A$, $I_{CC} = 5mA$

$$\frac{3.3V \times 0.2A}{5V \times (0.2A + 5mA)} \times 100 = 64\%$$

- Factor: The smaller the input/output voltage ratio, the lower is efficiency

◆ Thermal calculation

- $T_j = \text{Power Loss} \times \text{Thermal Resistance } \theta_{ja} + T_a$
 - Power Loss = $(V_{IN} - V_O) \times I_{IN}$
- EX: Above condition, $\theta_{ja} = 50^\circ\text{C/W}$, $T_a = 40^\circ\text{C}$
- $$\{(5V - 3.3V) \times (0.2A + 5mA)\} \times 50^\circ\text{C/W} + 40^\circ\text{C} = 57^\circ\text{C}$$
- At $T_{jmax} = 125^\circ\text{C}$, 68°C margin is given
- Make sure T_{jmax} is not exceeded
 - Factor: Heating increases as input/output voltage difference and I_O rise.

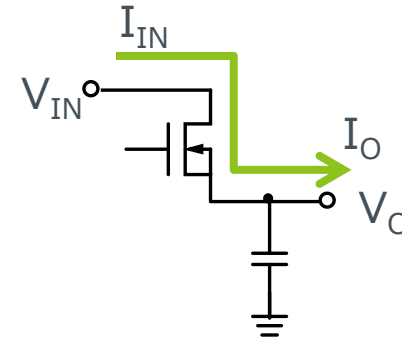


Is the efficiency of LDO really low?

If $V_{IN} = 3.6V$ at the left conditions,

$$\frac{3.3V \times 0.2A}{3.6V \times 0.205A} \times 100 = 89\%$$

Almost Same as Switching Regulators!

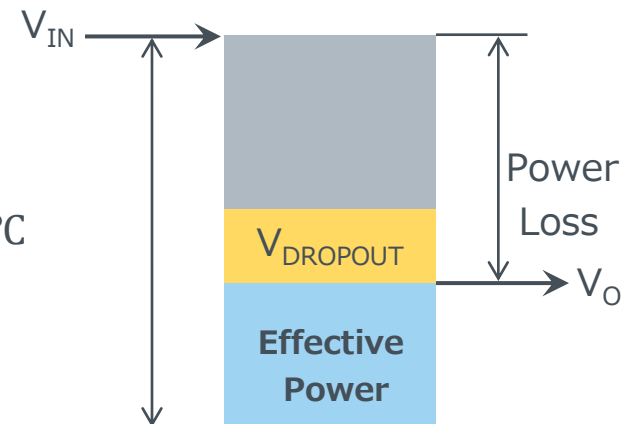

2. Switching Regulator Basics

- Types of Switching Regulators
- Advantages vs Disadvantages, and Comparison with Linear Regulator
- Operating Principles of Buck Converter
- Differences between Synchronous and Nonsynchronous Rectifying
- Efficiency Improvements at Light Load for the Synchronous Converter
- Control Methods (Voltage Mode, Current Mode, Hysteresis Control)
- Protective and Sequencing Functions
- Considerations on Switching Frequencies

Types of Switching Regulators

DC/DC Converter

Non Isolated

Non-synchronous

Synchronous


Isolated

Flyback

Forward

Push-Pull

Half/Full bridge

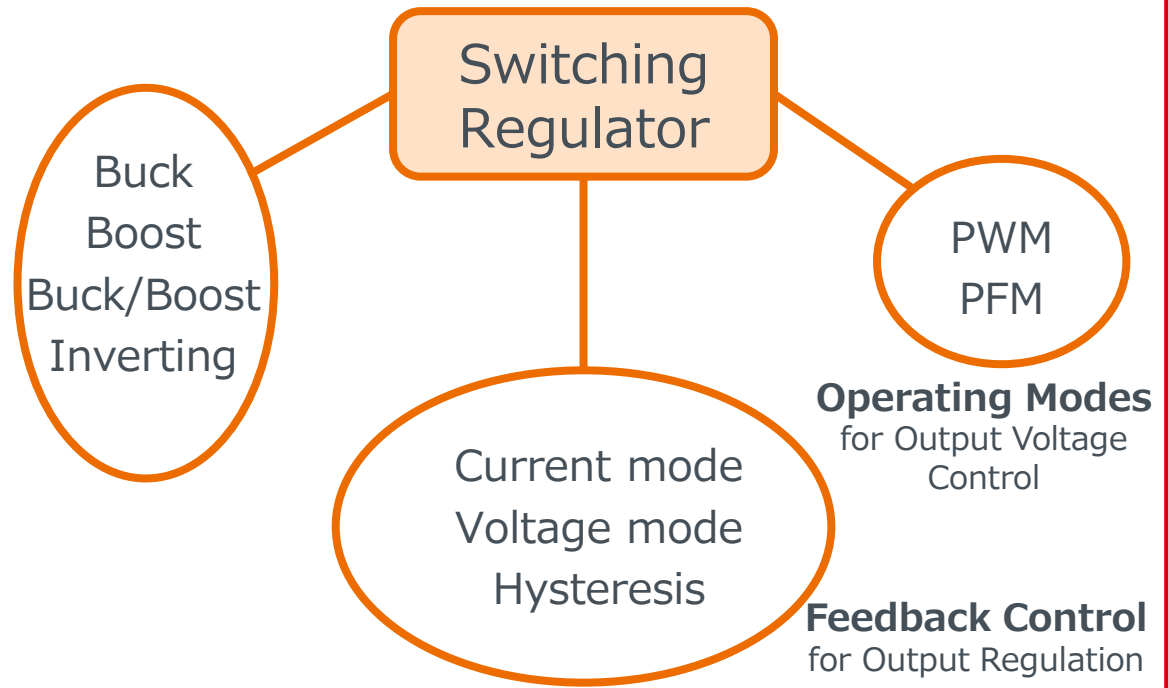

AC/DC Converter

Non isolated

Isolated

- **Application:** consumer, industrial, domestic, overseas. . .
- **Input/Output Conditions:** AC, DC, battery. . .
- **Requirements:** power, efficiency, accuracy. . .
- **Limitations:** size, cost, restrictions. . .

Comparison with Linear Regulator


Advantages

- ✓ Capable of Boost, Buck, Inverting and Buck/Boost
- ✓ High efficiency
- ✓ Low thermal dissipation
- ✓ Can handle a large output current
- ✓ Complicated design
- ✓ High parts count
- ✓ Switching noise and ripple exist
- ✓ Cost factor


	Linear Regulator	Switching Regulator
Buck Boost Buck/Boost Inverting	Possible Impossible Impossible Impossible	Possible Possible Possible Possible
Efficiency	V_O/V_{IN} Mostly low	Approx. 95% Usually high
Output Power	Generally several watts Depending on thermal design	Large power possible
Noise	Low	Switching noise exists
Design	Simple	Complicated
BOM	Low count	High count
Cost	Low	Relatively high

Operating Principles of Buck Converter

Buck Conversion Operating Principles

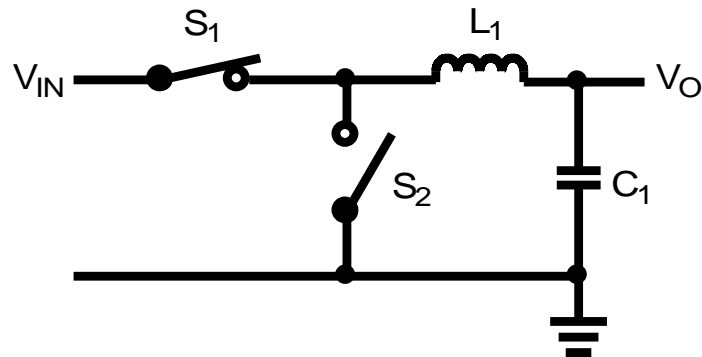


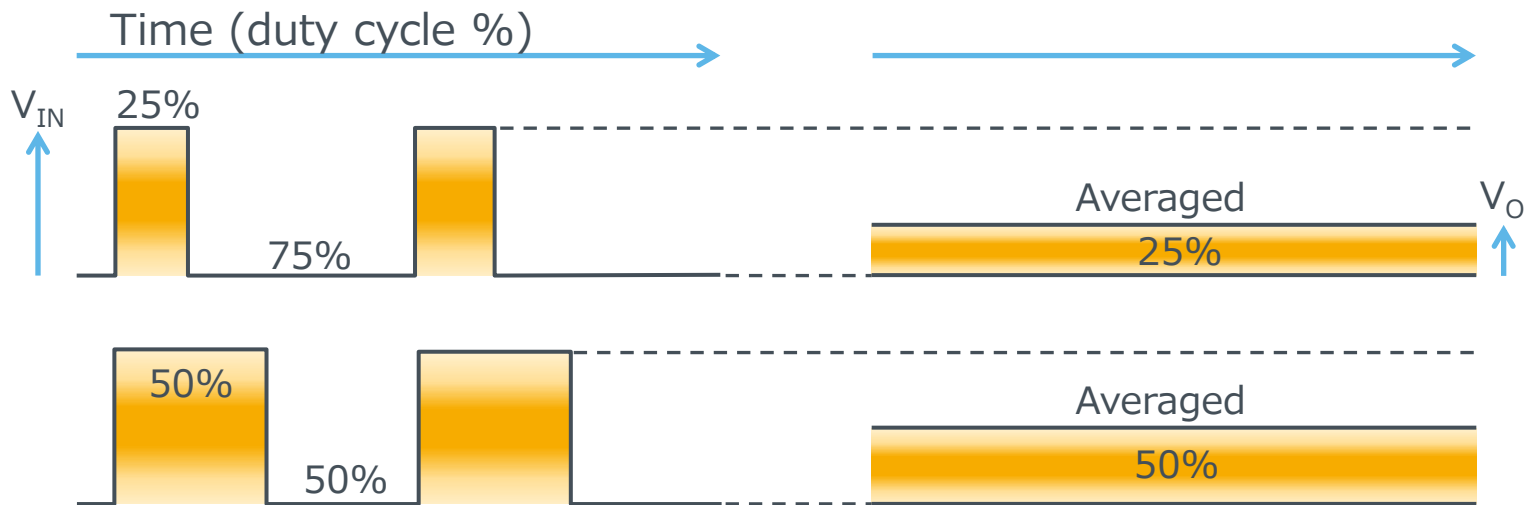
- When S1 is on and S2 off, V_{IN} is applied to $L1$.
- When S1 is off and S2 on, $L1$ is connected to GND.
- V_{IN} (DC) is converted to V_{IN}/GND level pulses.
- The voltage is averaged in $C1$ and converted to DC.





Operating Principles of Buck Converter

Basic Circuit for Nonsynchronous (diode) DC/DC Conversion

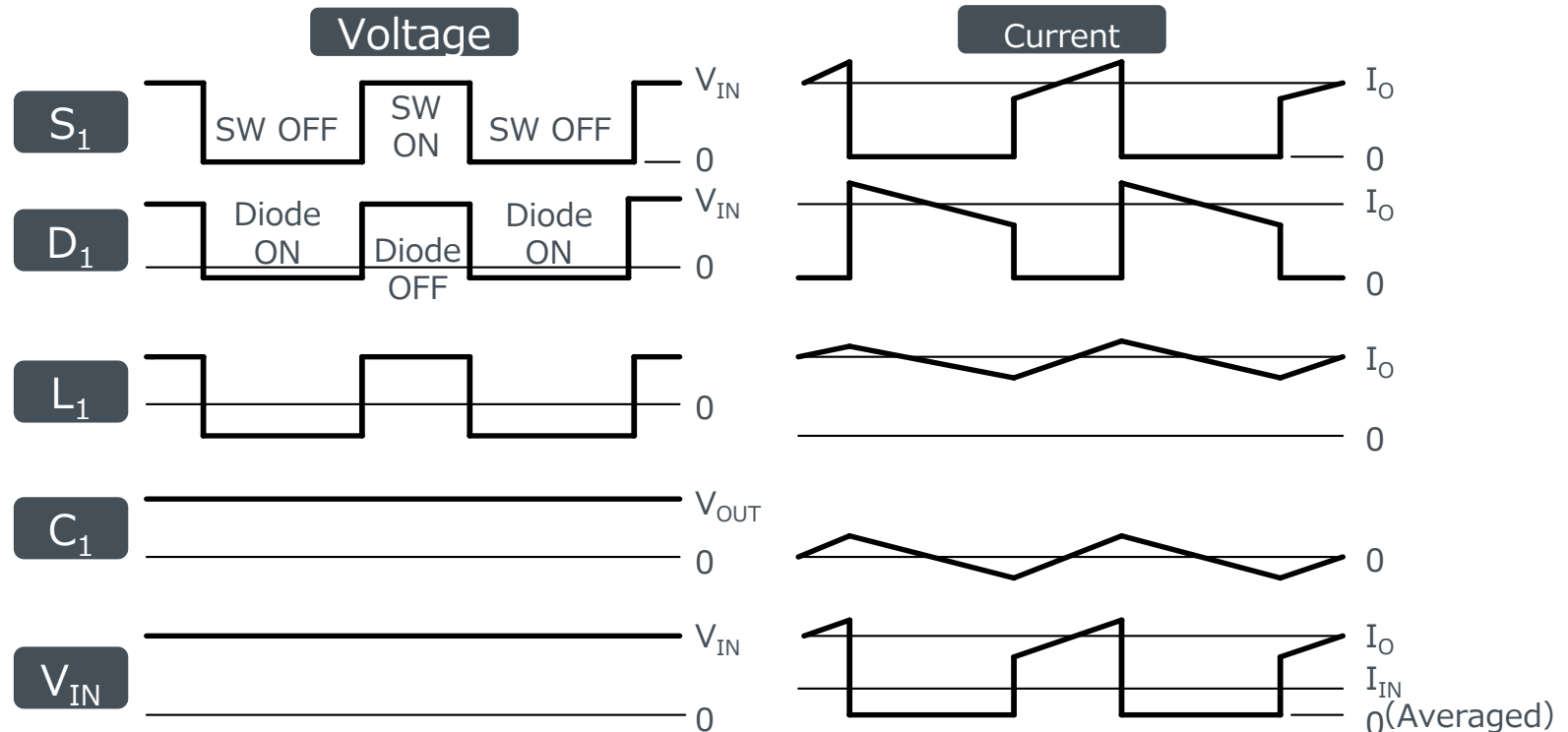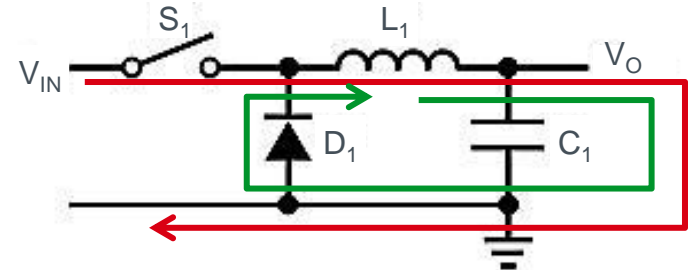
- S_1 : normal transistor element
- D_1 : denotes as S_2 in the preceding page
- Red line: a current path when S_1 is on;
green line, when S_1 is off



Operating Principles of Buck Converter

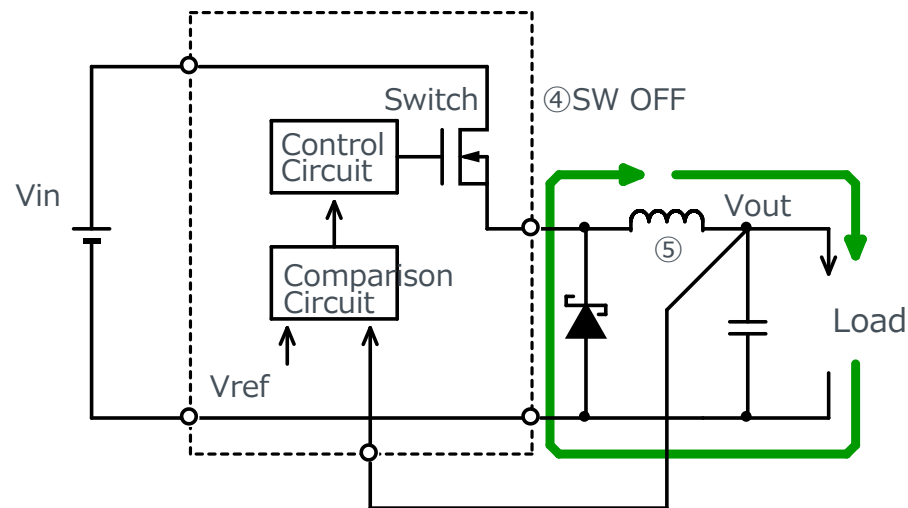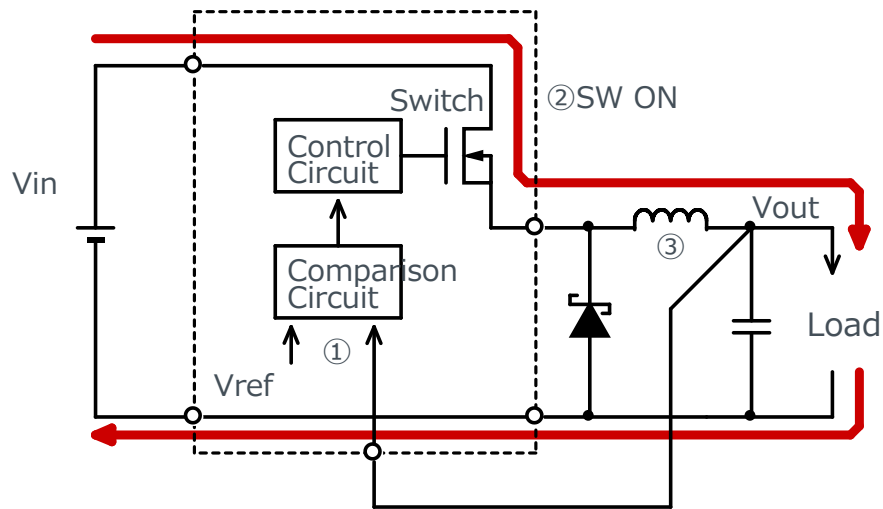


- ① The comparison circuit (error amp) compares the output voltage with the reference voltage to determine if it is equal to a set voltage.
- ② If the output voltage is less than the set voltage, the switch (MOSFET) is turned on, supplying power from the input to the output.
- ③ In this case, magnetic energy is accumulated in the inductor.
- ④ When the output voltage exceeds the set voltage, the switch is turned off.
- ⑤ The magnetic energy stored in the inductor is supplied to the output load in the form of current, and it returns to the inductor.
- ⑥ When the magnetic energy in the inductor is depleted and the output voltage declines, the switch turns on again.

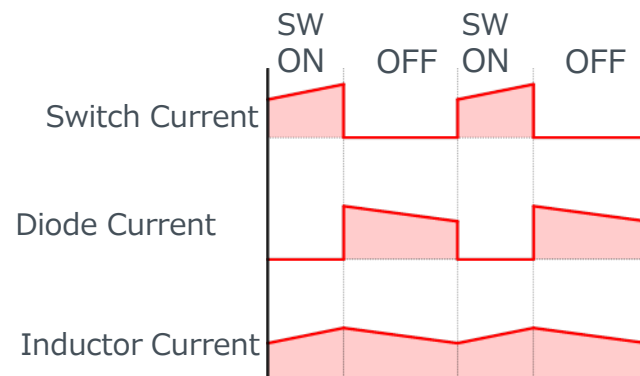


Differences between Synchronous & Nonsynchronous

Nonsynchronous (diode) Rectifying

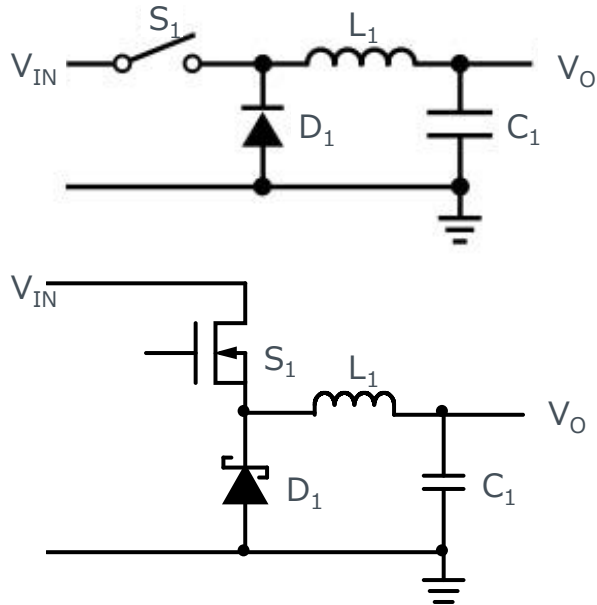

Synchronous rectifying

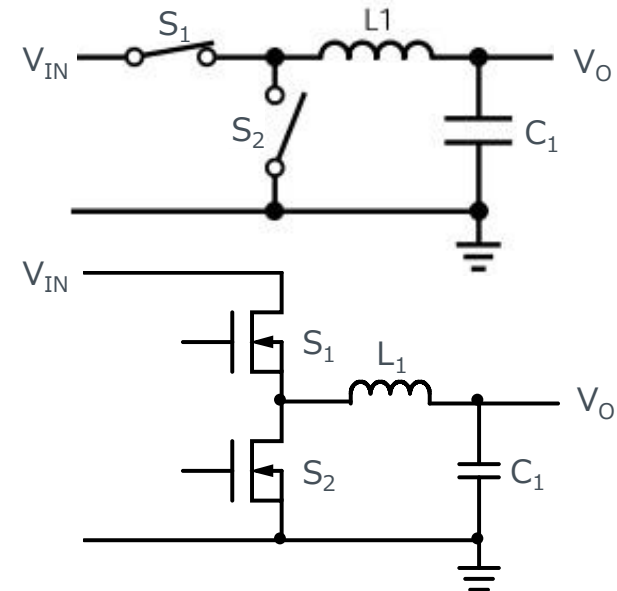


- When S_1 is on, no current flows to D_1 (off)
- When S_1 is off, a forward current flows to D_1 (on)
- In an actual circuit, S_1 comprises a transistor, and D_1 a Schottky diode
- In efficiency, the nonsynchronous rectifying type trails the synchronous type
- The circuit is relatively simple

- When S_1 is on, S_2 is turned off
- When S_1 is off, S_2 is turned on
- Same current path as nonsynchronous, but the switches are controlled by the control circuit
- A transistor is actually used for the switch
- High efficiency, but it requires special provisions to boost its efficiency at low load
- More complex circuitry to the nonsynchronous

Differences between Synchronous & Nonsynchronous

Nonsynchronous (diode) Rectifying

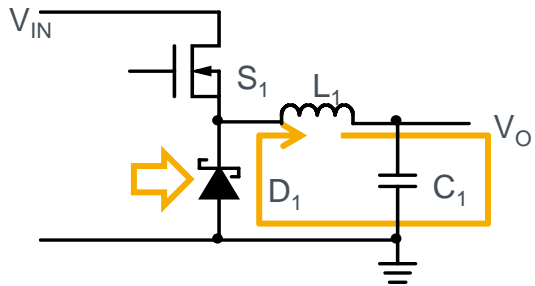


V_F of D1 presents a problem when step-down ratio is high




- When the step-down ratio is high, D1 has a long conduction time
- A low V_O value increases dropout by V_F of D1

Synchronous rectifying

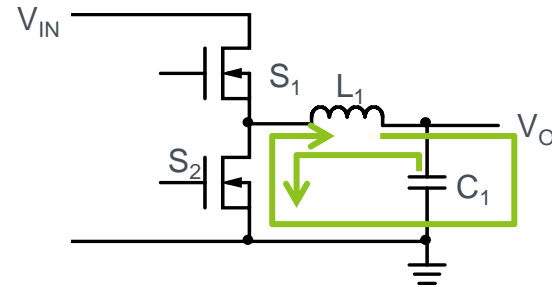

Operation at light load

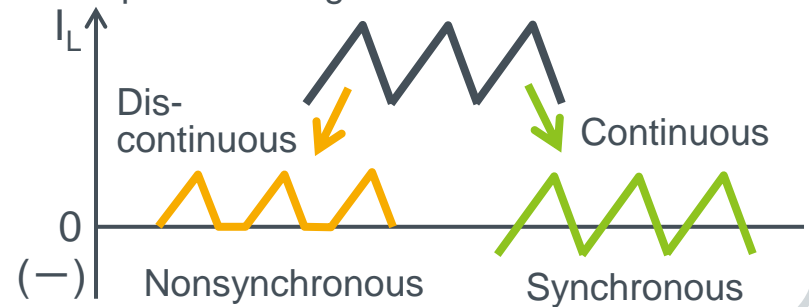

- Under light load, the inductor current remains at 0A for some time
- In the nonsynchronous, a current flows through the diode only in one direction, resulting in a discontinuous operation and a ringing condition
- In the synchronous, a current can flow in a reverse direction in the transistor, for a continuously regulation, but lower efficiency


Efficiency Improvements at Light Load

1. Addition of a Discontinuous Mode

Improving the efficiency of the synchronous rectifying involves the addition of a function that operates in discontinuous mode during the light load state.

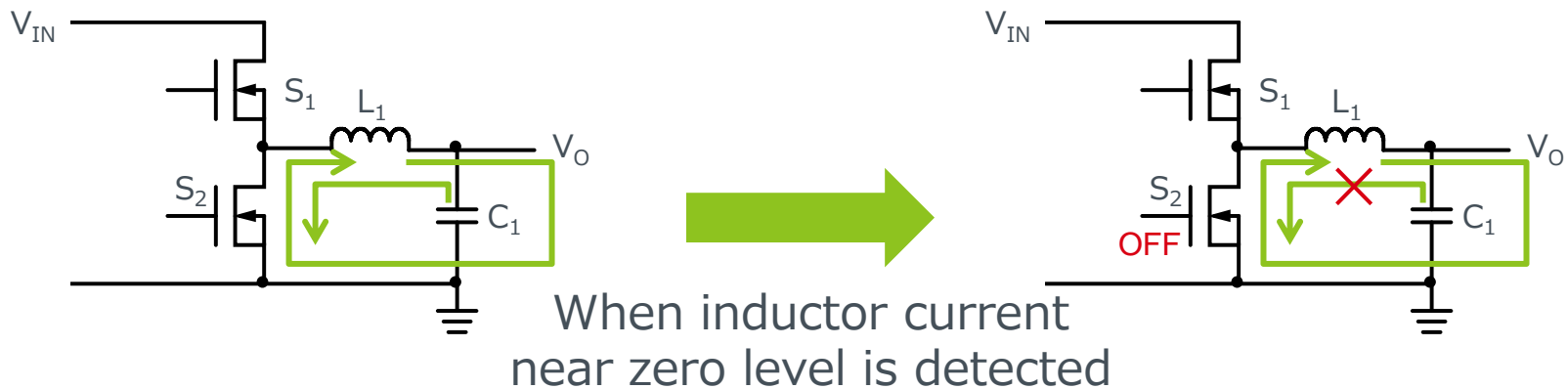- i. Detect the inductor current falling to almost zero
- ii. Turned off the low-side transistor
- iii. Prevent any reverse current flow



During discontinuous mode at light load, it makes the switching speed reduce and increases the ripple voltage in some cases.




Efficiency Improvements at Light Load

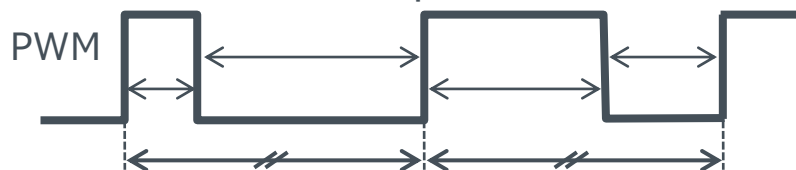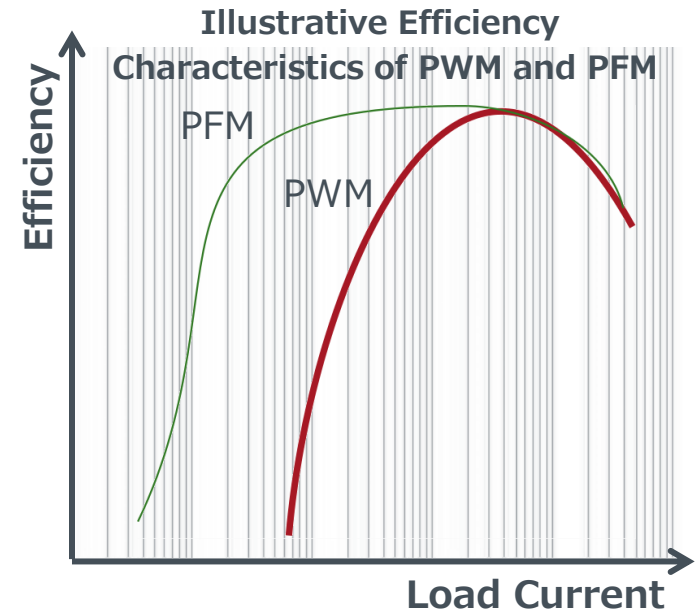2. Switching from PWM mode to PFM mode

- In pulse-width modulation (PWM), the frequency is constant, and duty cycles are adjusted
 - ✓ Because the frequency remains fixed even during light load conditions, switching loss reduces the efficiency
 - ✓ The fixed frequency facilitates the noise filtering
- In pulse-frequency modulation (PFM), the on- (or off-time) is fixed, and the off- (or on-) time is adjusted
 - ✓ Reduced-frequency operations cut switching loss
 - ✓ The unknown frequency makes noise-filtering difficult, with the result that some noise ends up in an audible band



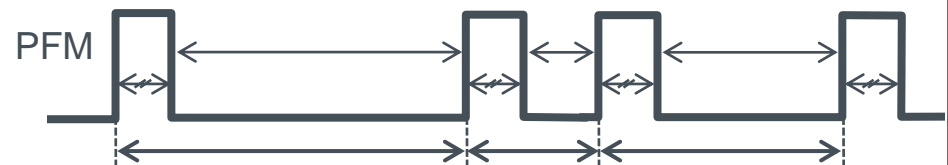The cycle remains constant with a variable on/off time ratio




The on-time is constant with a variable off-time = cycle also fluctuates

Control Methods


Voltage Mode Control

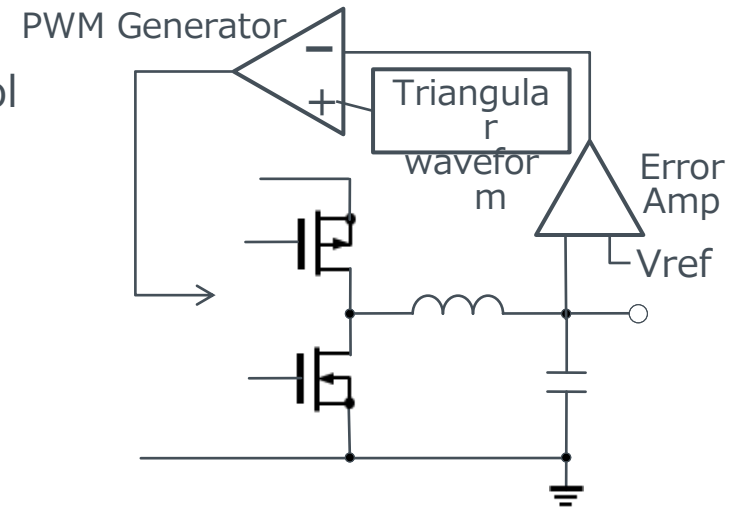- ✓ A voltage-only feedback loop makes control simple
- ✓ The ability to control shorter on-time
- ✓ High noise tolerance
- ✓ Complex phase compensation circuitry



Current mode control

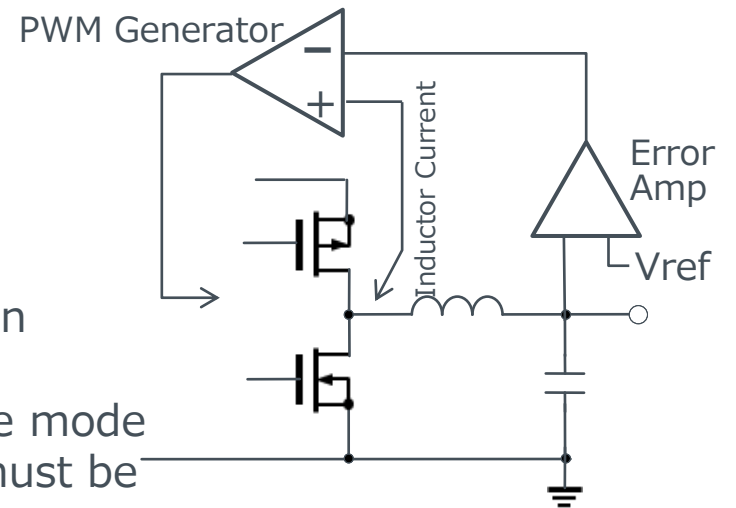- ✓ Modified voltage mode control
- ✓ Detects and uses circuit inductor current instead of triangular waves
- ✓ High stability of the feedback loop
- ✓ Substantially simplified phase compensation circuit design
- ✓ Faster load transient response than voltage mode
- ✓ Noise to current detection feedback loop must be addressed



Hysteresis (ripple) Control

- ✓ Directly monitors output voltage with a comparator
- ✓ Extremely fast load transient response
- ✓ Highly stable feedback loop
- ✓ Eliminates the need for phase compensation
- ✓ Variable switching frequencies
- ✓ Large jitter
- ✓ Requires a capacitor with a large ESR value to detect ripples


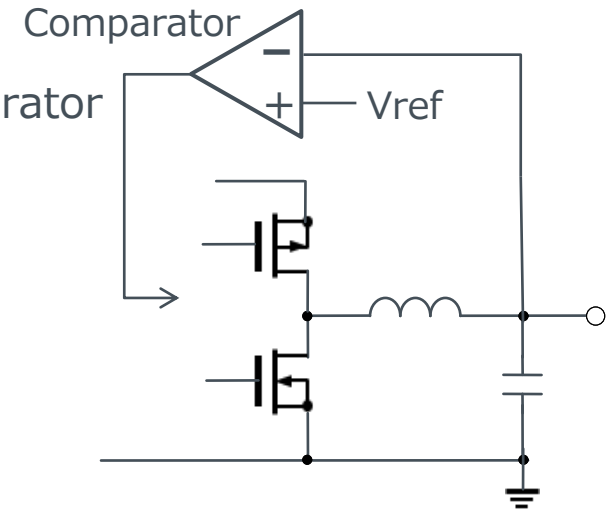


Illustration of Hysteresis Control

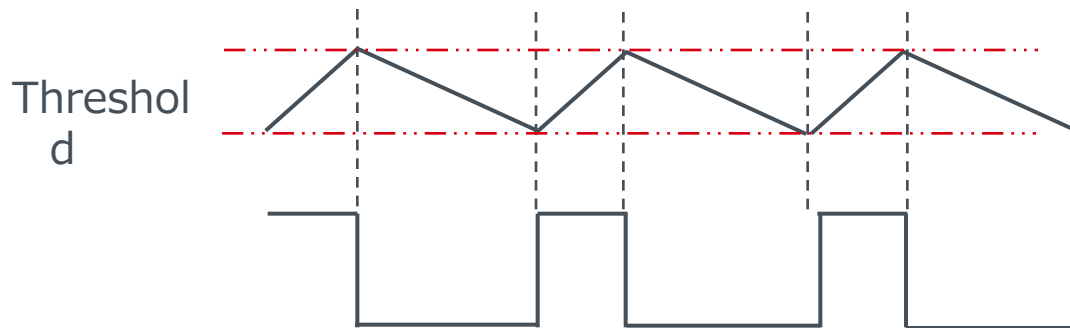


Output voltage (output ripple)

Switching on/off

Protective Functions


◆ Thermal Shut Down (TSD)

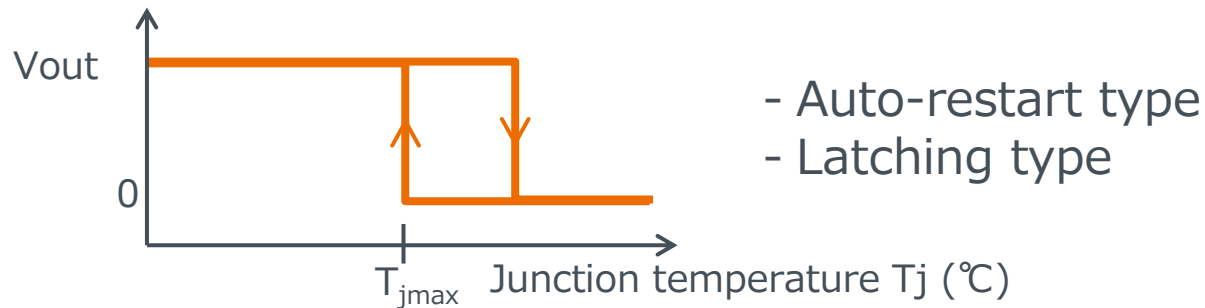Operation ceases when IC junction temperature T_j reaches the maximum rating $T_{jmax} \pm \alpha$




◆ Under Voltage Lock Out (UVLO)

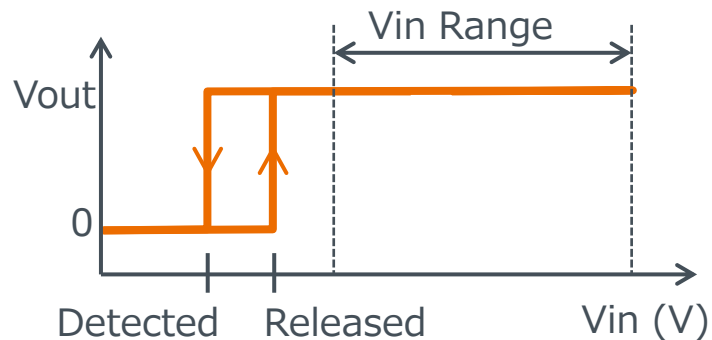Shuts down when input voltage falls below a preset level




Protective Functions

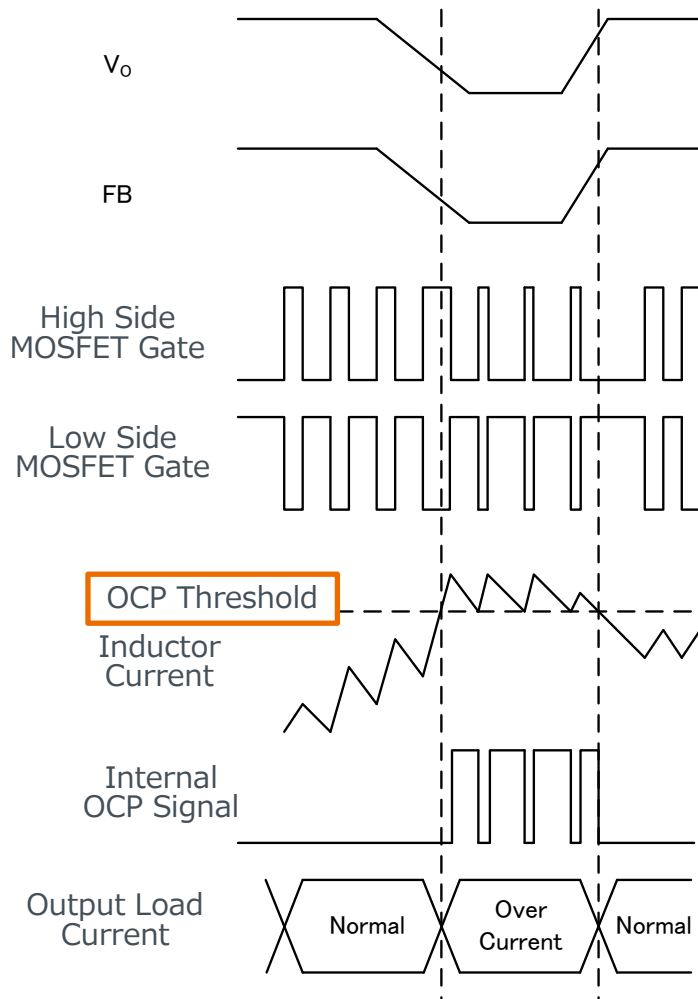- ◆ **Over Current Protection (OCP)**
Limit the current when output current exceeds a limit value





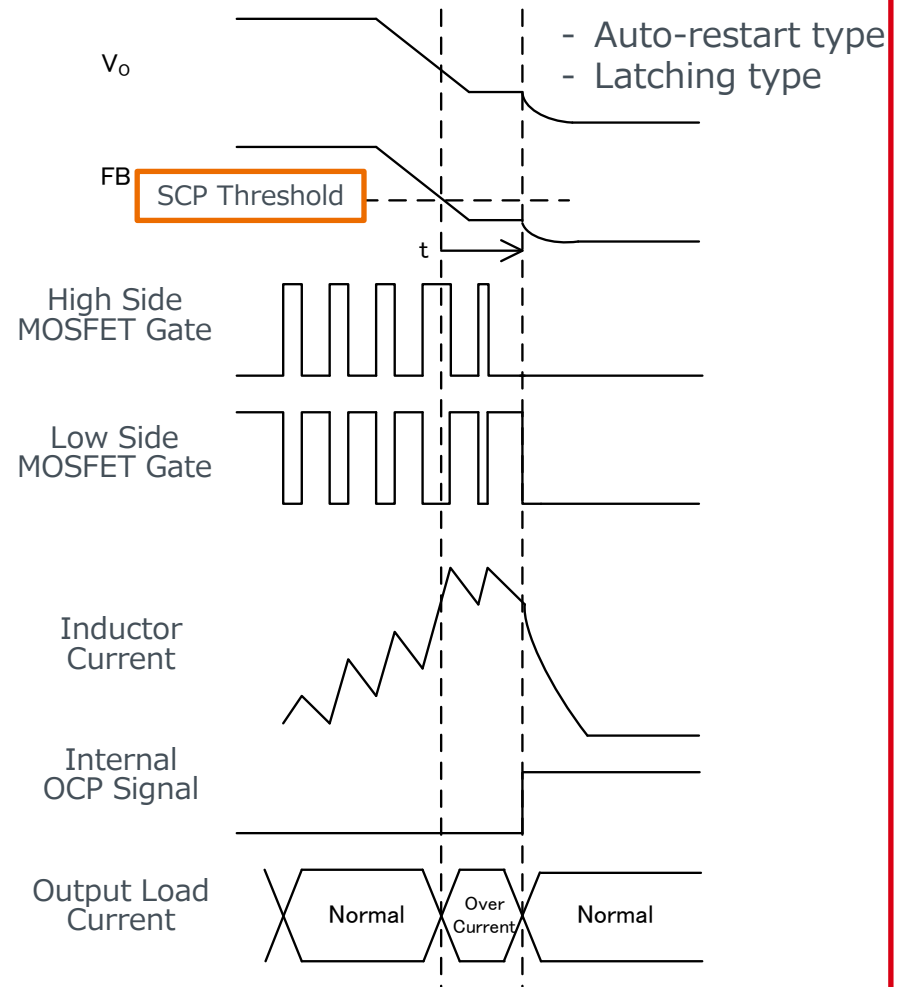- ◆ **Short Circuit Protection (SCP)**
Shuts off operation when output voltage falls below a set level



◆ Over-Voltage Protection (OVP)

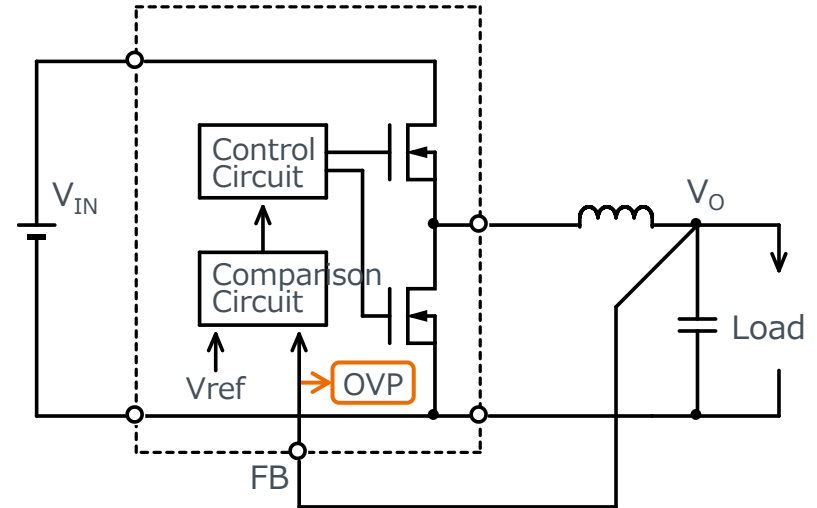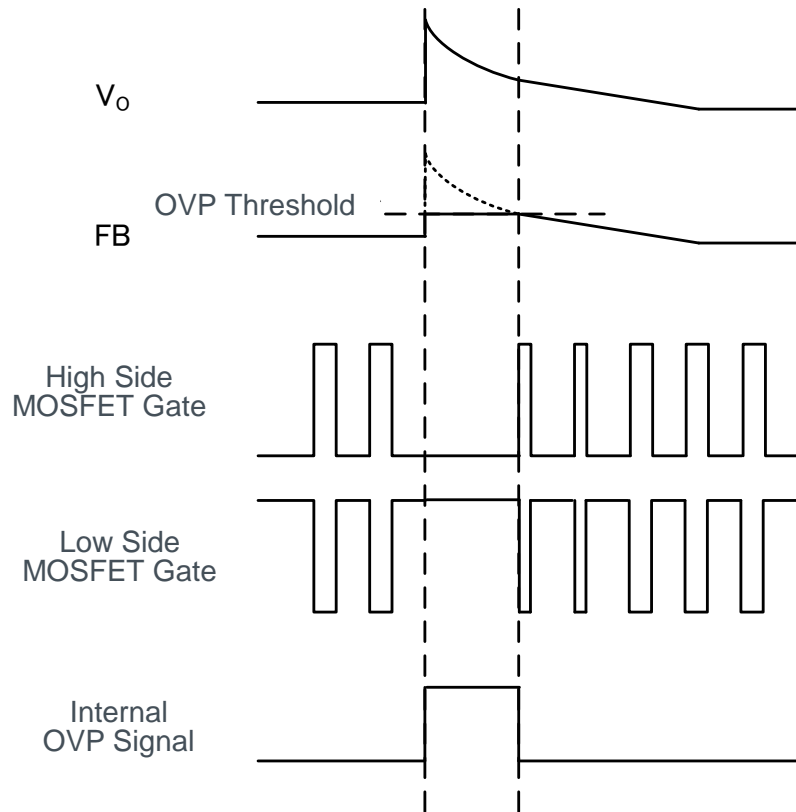
Operation stops when a voltage on output exceeds a set level



Sequencing Functions


Shutdown: On/off the operation of internal control circuit (same as “Enable” function)

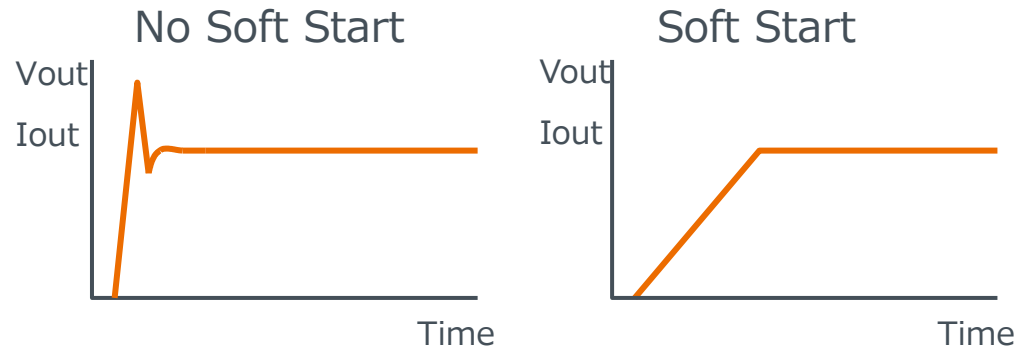Soft start: Prevent inrush current at startup slowly to rise V_{out}






Power-good output: Raise a flag when the output reaches a set voltage level
 Notify other devices the power supply has started up

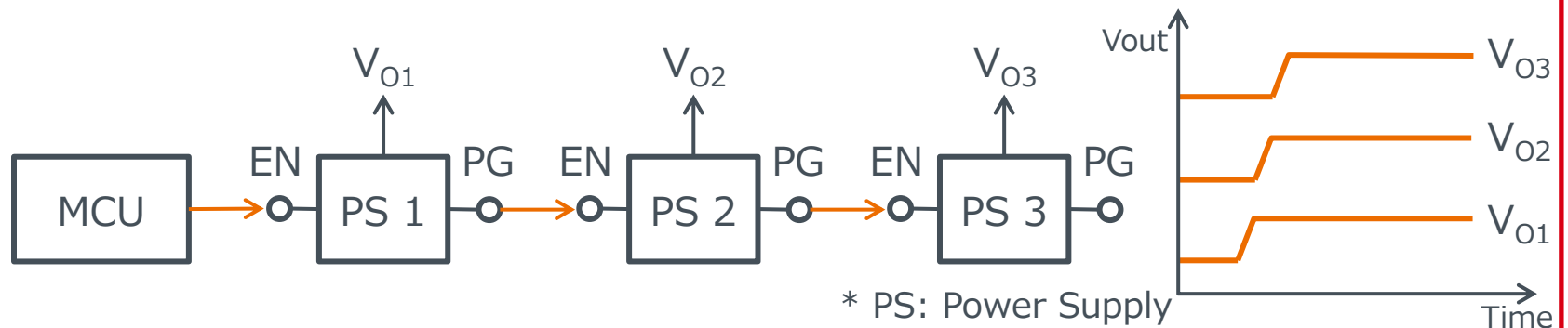Construct a startup sequence for multiple power supply with the enable function



Sequencing Functions

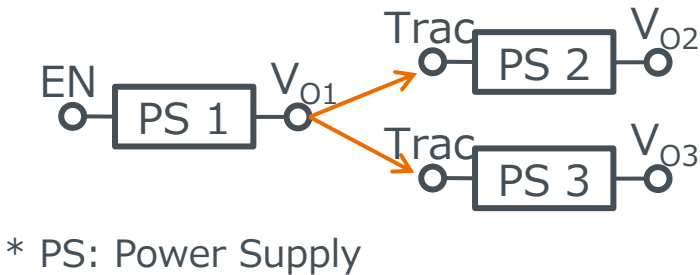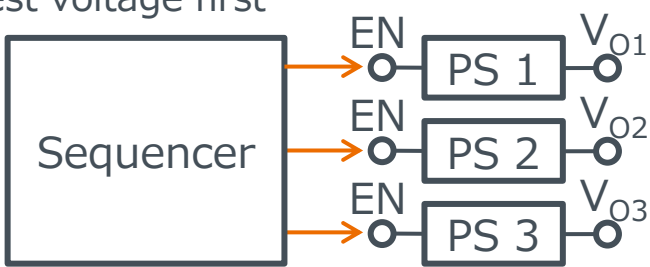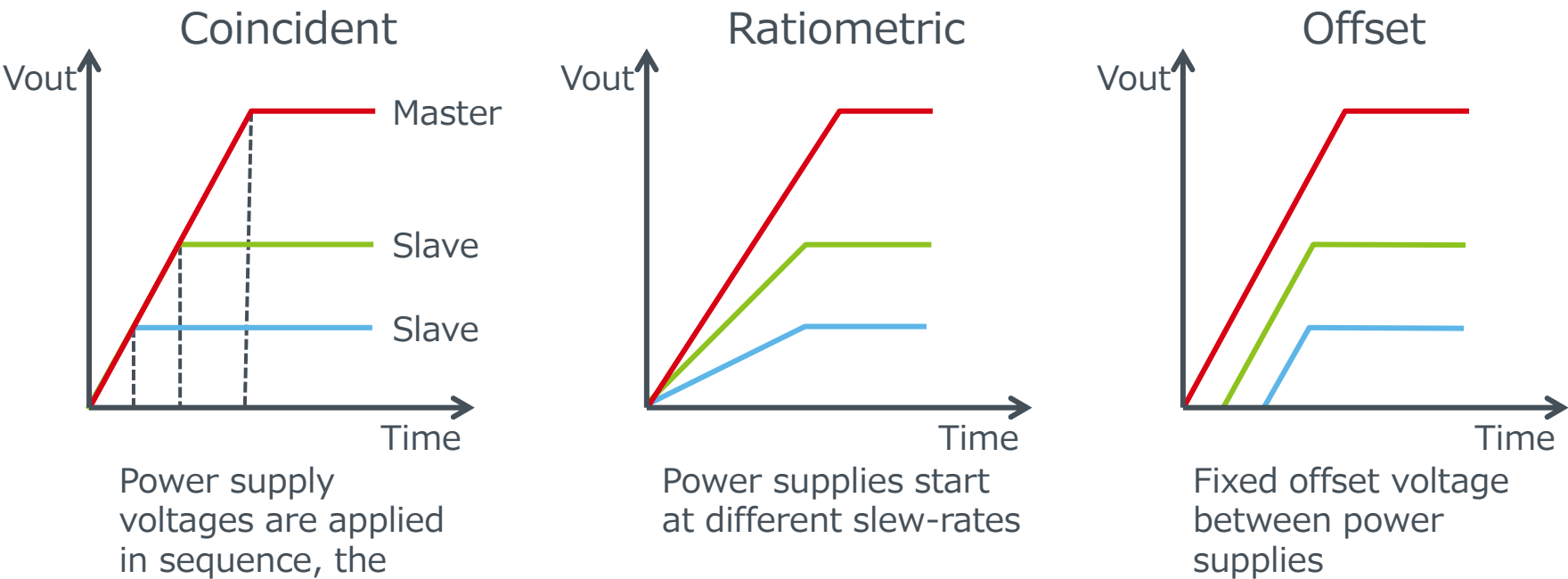Tracking: Set the sequence and timing of multiple power supplies at start up
 There are 3 types



Considerations on Switching Frequencies

Tradeoff between Efficiency and Size

Increasing the switching frequency:


- permits a reduction in size of external inductor and capacitor
- reduces efficiency due to switching loss
- reduces ripples, and tends to cut noise as well, and
- improves transient response.

Switching Frequency	Up to hundreds kHz	1 MHz or higher
Parts Size	Large	Small
Efficiency	Increases	Diminishes
Noise	Large	Small
Ripple	Large	Small
Transient Response	Slow	Fast

AGENDA

1. Linear Regulator Basics
 - Operating Principles
 - Types and Circuit Configuration
 - Advantages vs Disadvantages, and Applications
 - Important Specifications
 - Efficiency and Thermal Calculation
2. Switching Regulator Basics
 - Types of Switching Regulator
 - Advantages vs Disadvantages, and Comparison with Linear Regulator
 - Operating Principles of Buck Converter
 - Differences between Synchronous and Nonsynchronous Rectifying
 - Efficiency Improvements at Light Load for the Synchronous Converter
 - Control Methods (Voltage Mode, Current Mode, Hysteresis Control)
 - Protective and Sequencing Functions
 - Considerations on Switching Frequencies

Web Site for Linear Regulator & Switching Regulator



COMPANY | CSR | NEWS | MYROHM LOGIN |

Products Applications Sales & Support

ICs

- Memory
- Amplifiers & Linear
- Power Management
- Clocks & Timers
- Switch & Multiplexer & Logic
- Data Converter
- Sensors & MEMS
- Display Drivers
- Motor / Actuator Drivers
- Interface
- Communication LSI (LAPIS)
- Audio & Video
- Speech Synthesis LSI (LAPIS)
- Microcontrollers (LAPIS)

Discrete Semiconductors

- Transistors
- Diodes

Passive Components

- Resistors
- Tantalum Capacitors

Modules (Modules)

- Power Modules
- Wireless Modules
- Contact Interconnects
- Printed Circuit Boards
- Batteryless ICs

Opto Electronics

- LED
- LED Displays
- Laser Diodes
- Optical Sensors
- IrDA Infrared
- Remote Controls

Click Here

LINEAR REGULATORS (851)

ROHM offers a wide lineup of general-purpose 3-pin regulators featuring low power consumption, high current capability, and high voltage resistance, making them ideal for mobile phones, automotive systems, consumer electronics, and commercial/industrial equipment.

Automotive Regulator Selection Guide



- Single-Output LDO Regulators (729)
- Multi-Output LDO Regulators (14)
- Standard Voltage Regulators (89)
- LDO Regulators with Watch-Dog Timer (5)
- LDO Regulators with Voltage Detector (5)
- Voltage Trackers (2)
- Linear Regulators for DDR-SDRAM (7)

SWITCHING REGULATORS (192)

ROHM's switching regulator series (DC/DC converter) are available with or without integrated FET (boost/buck/boost-buck) and from single-channel to multi-channel system power supply configurations for broad compatibility.

DC/DC Converter IC Support Page **Evaluation Boards Order Page** **DC/DC Converter Selection Guide** **Automotive Regulator Selection Guide**

- Switching Regulators (Integrated FET) (150)
- Switching Regulators (Controller) (20)
- Multi-Output Switching Regulators (15)



<http://www.rohm.com/>

